

(Please write your Exam Roll No.)

Exam Roll No.

END TERM EXAMINATION

SECOND SEMESTER [BCA] MAY-JUNE 2009

Paper Code: BCA-106

Subject: Digital Electronics

Paper Id: 20106

(Batch: 2005-2008)

Time : 3 Hours

Maximum Marks :75

Note: Q1. is compulsory. Attempt one question from each part.

- Q1. (a) State and prove De-Morgan's theorem. (5)
 (b) Describe and compare Register, Main Memory and Secondary Memory. (5)
 (c) What are the drawbacks of S-R Flip-flop? How are they removed in J-K flip-flop? (5)
 (d) Perform the following conversions: (5)
 (i) $(AB.08)_{16} = ()_{10}$
 (ii) $(670.04)_8 = ()_{16}$
 (e) Design full-subtractor using NAND Gate only. (5)

PART-A

- Q2. (a) Realize (i) $Y = A+BC\bar{D}$ using NOR Gates only. (6)
 (ii) $Y = (A+C)(A+\bar{D})(A+B+\bar{C})$ using NAND Gates only.
 (b) Express the function $Y = A+\bar{B}C+B\bar{D}$ in (6.5)
 (i) Canonical SOP form
 (ii) Canonical POS form
- Q3. (a) Using the K-Map method, simplify the following Boolean function (6.5)
 $F = \sum_m (0,2,3,6,7) + \sum_n (8, 10, 11, 15)$
 And obtain (i) minimal SOP and (ii) minimal POS expressions
 (b) If $\bar{A}B + \bar{C}\bar{D} = 0$, then by using Boolean algebra's laws and properties prove that: (6)
 $\bar{A}B + \bar{C}(A+\bar{D}) = \bar{A}\bar{B} + \bar{B}\bar{D} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$

PART-B

- Q4. (a) Explain Binary Multiplier. (6)
 (b) Show how a full-adder can be converted to a full-subtractor with the addition of an inverter circuit. (6.5)
- Q5. (a) What are MUX & DEMUX? Implement the following function using Multiplexer: (6.5)
 $F = \sum_m (0,1,3,4,8,9,13,15)$
 (b) Design a code converter to convert Grey code into Binary code. (6)

PART-C

- Q6. (a) Define flip flop. Realize JK flip-flop using D-flip-flop. (6)
 (b) Differentiate between combinational and sequential circuits. Explain the Race-Around condition and how can it be eliminated in Master-Slave JK Flip Flop? (6.5)
- Q7. (a) What are shift Registers? How are they different from Data Registers? The content of a 4-bit shift register is initially 1101. The register is shifted 6 times to the right with the serial input being 101101. What will be the final content of the register after all the 6 shifts are over? (6.5)
 (b) Explain in detail the construction and working of Universal/Bidirectional shift register. (6)

PART-D

- Q8. (a) Design a mod-10 counter to count in Grey code using D-flip flop. (6)
 (b) What is a Ripple Counter? Draw the wave forms to explain how this circuit can be used as a "Frequency Divider". (6.5)
- Q9. (a) What is a RAM? State the differences between Static RAM and Dynamic RAM. (6)
 (b) What is a ROM? State the differences among ROM, PROM, EPROM and EEPROM. (6.5)